

NEC 304

STLD

Lecture 6

More Boolean Algebra

Rajeev Pandey

Department Of ECE

rajeevvce2007@gmail.com


Overview

- **Expressing Boolean functions**
- **Relationships between algebraic equations, symbols, and truth tables**
- **Simplification of Boolean expressions**
- **Minterms and Maxterms**
- **AND-OR representations**
 - **Product of sums**
 - **Sum of products**

Boolean Functions

- Boolean algebra deals with binary variables and logic operations.
- Function results in binary 0 or 1


x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

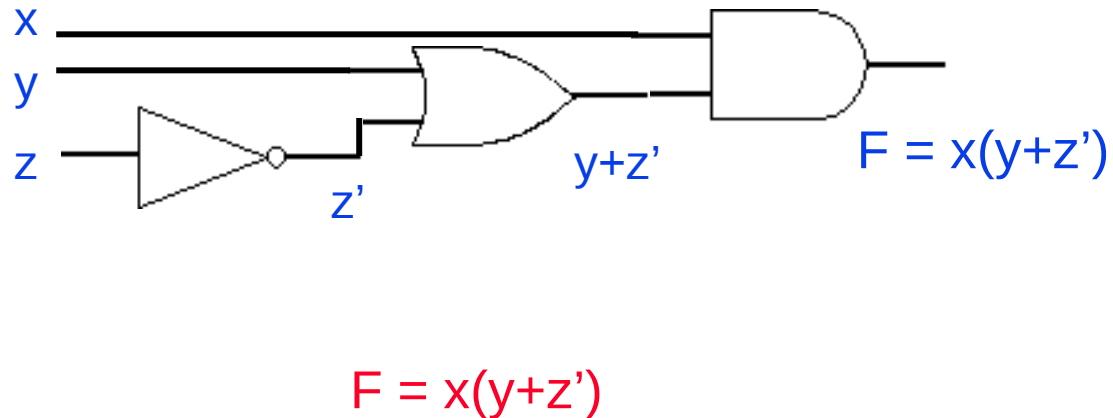

Boolean Functions

- ° Boolean algebra deals with binary variables and logic operations.
- ° Function results in binary 0 or 1


x	y	z	xy	yz	G
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	1	1

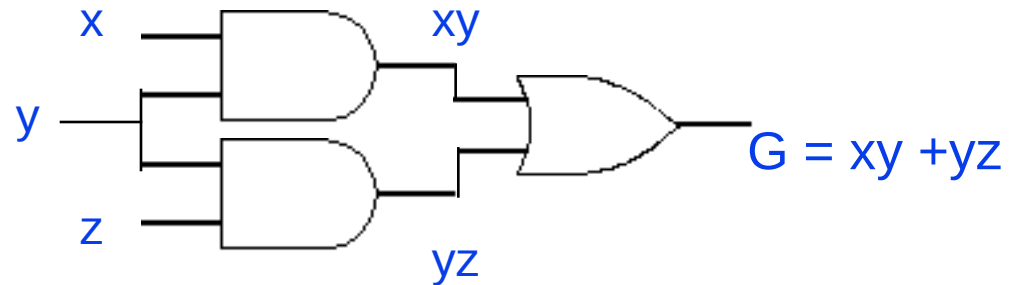

We will learn how to transition between equation, symbols, and truth table.

Representation Conversion

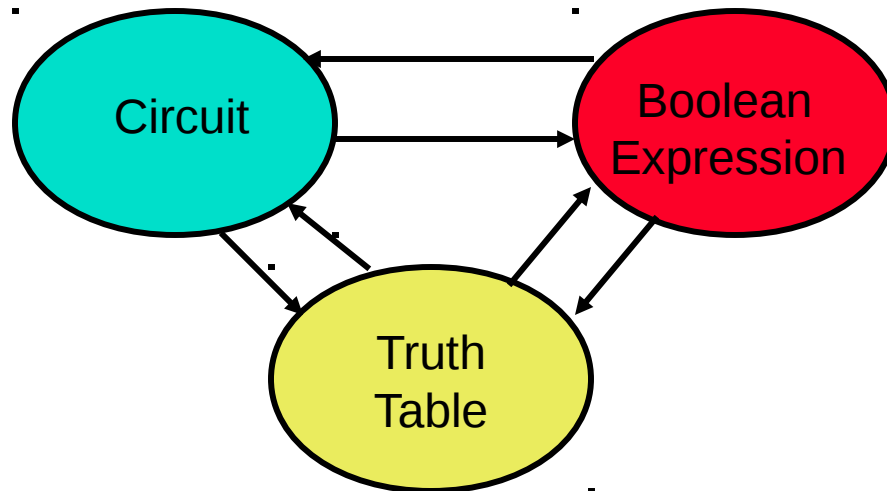
- Need to transition between boolean expression, truth table, and circuit (symbols).
- Converting between truth table and expression is easy.
- Converting between expression and circuit is easy.
- More difficult to convert to truth table.



Truth Table to Expression

- Converting a truth table to an expression
 - Each row with output of **1** becomes a **product term**
 - **Sum** product terms together.

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

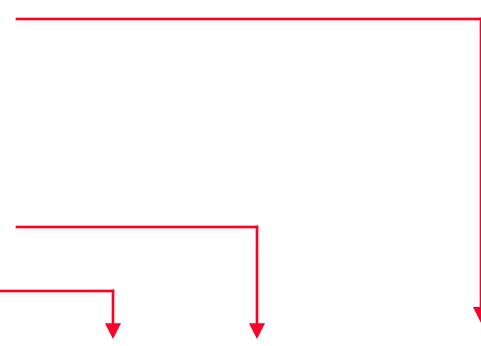

$xyz + xyz' + x'yz$


*Any Boolean Expression can be represented in **sum of products form**!*

Equivalent Representations of Circuits

- All three formats are equivalent
- Number of 1's in truth table output column equals AND terms for Sum-of-Products (SOP)

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$G = xyz + xyz' + x'yz$$

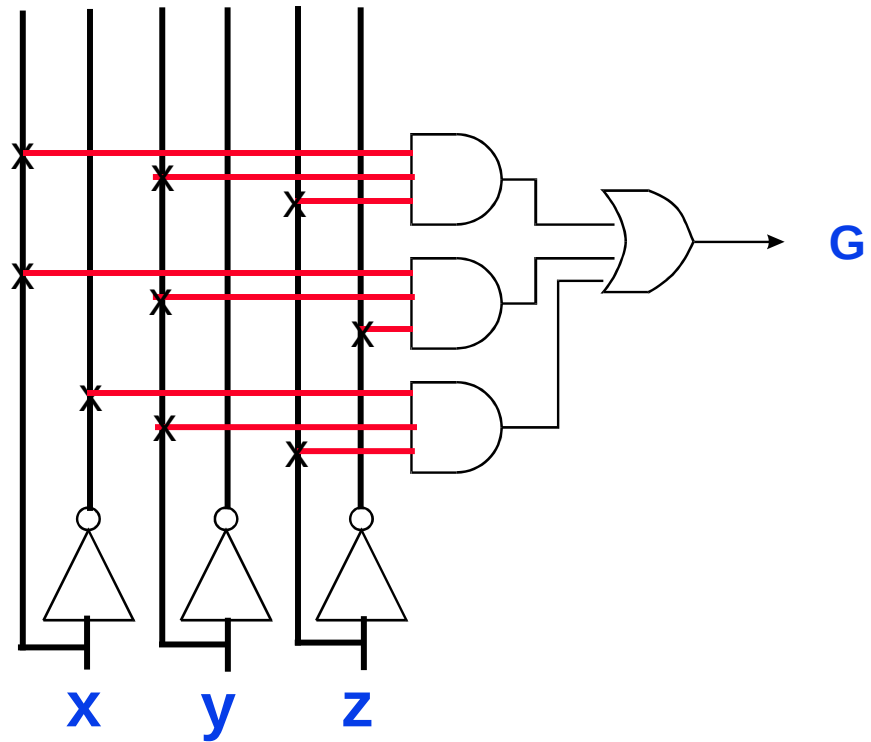


Reducing Boolean Expressions

- Is this the smallest possible implementation of this expression? **No!** $G = xyz + xyz' + x'yz$
- Use Boolean Algebra rules to reduce complexity while preserving functionality.
- Step 1: Use Theorem 1 ($a + a = a$)
 - So $xyz + xyz' + x'yz = xyz + xyz + xyz' + x'yz$
- Step 2: Use distributive rule $a(b + c) = ab + ac$
 - So $xyz + xyz + xyz' + x'yz = xy(z + z') + yz(x + x')$
- Step 3: Use Postulate 3 ($a + a' = 1$)
 - So $xy(z + z') + yz(x + x') = xy.1 + yz.1$
- Step 4: Use Postulate 2 ($a . 1 = a$)
 - So $xy.1 + yz.1 = xy + yz = xyz + xyz' + x'yz$

Reduced Hardware

- Implementation
 - Reduced equation requires less hardware!
- Same function implemented!

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

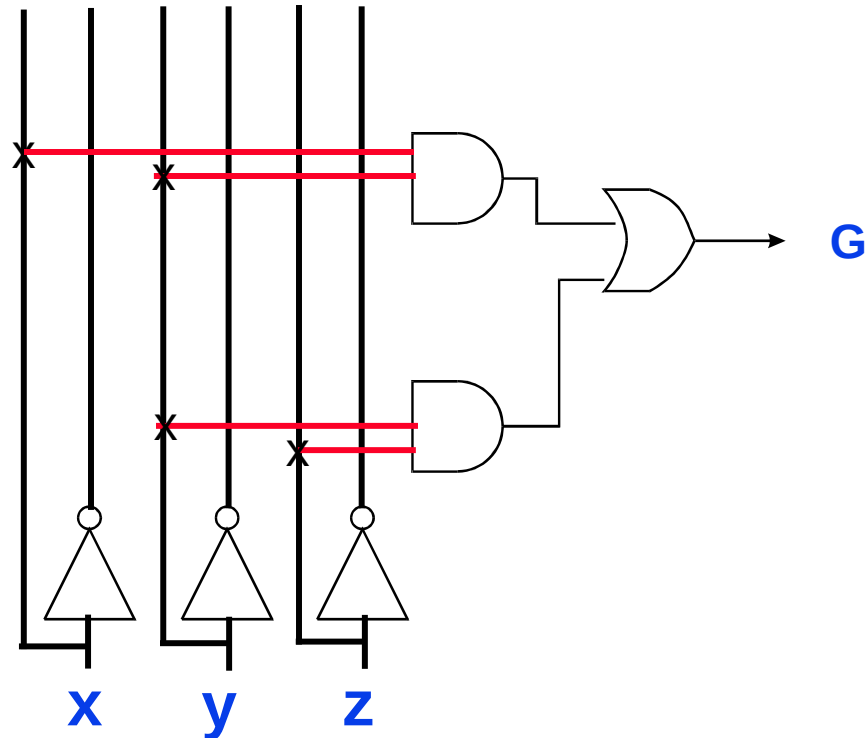

$$G = xyz + xyz' + x'yz = xy + yz$$

Minterms and Maxterms

- ° Each variable in a Boolean expression is a **literal**
- ° Boolean variables can appear in normal (**x**) or complement form (**x'**)
- ° Each AND combination of terms is a minterm
- ° Each OR combination of terms is a maxterm

For example:
Minterms

x	y	z	Minterm	
0	0	0	$x'y'z'$	m_0
0	0	1	$x'y'z$	m_1
...				
1	0	0	$xy'z'$	m_4
...				
1	1	1	xyz	m_7

For example:
Maxterms

x	y	z	Maxterm	
0	0	0	$x+y+z$	M_0
0	0	1	$x+y+z'$	M_1
...				
1	0	0	$x'+y+z$	M_4
...				
1	1	1	$x'+y'+z'$	M_7

Representing Functions with Minterms

- Minterm number same as row position in truth table (starting from top from 0)
- Shorthand way to represent functions

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$G = xyz + xyz' + x'yz$$



$$G = m_7 + m_6 + m_3 = \Sigma(3, 6, 7)$$

Complementing Functions

- Minterm number same as row position in truth table (starting from top from 0)
- Shorthand way to represent functions

x	y	z	G	G'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

$$G = xyz + xyz' + x'yz$$

$$G' = (xyz + xyz' + x'yz)' =$$

Can we find a simpler representation?

Complementing Functions

◦ Step 1: assign temporary names

- $b + c \rightarrow z$

$$G = a + b + c$$

- $(a + z)' = G'$

$$G' = (a + b + c)'$$

◦ Step 2: Use DeMorgans' Law

- $(a + z)' = a' \cdot z'$

◦ Step 3: Resubstitute **(b+c)** for **z**

- $a' \cdot z' = a' \cdot (b + c)'$

◦ Step 4: Use DeMorgans' Law

$$G = a + b + c$$

- $a' \cdot (b + c)' = a' \cdot (b' \cdot c')$

$$G' = a' \cdot b' \cdot c' = a'b'c'$$

◦ Step 5: Associative rule

- $a' \cdot (b' \cdot c') = a' \cdot b' \cdot c'$

Complementation Example

- Find complement of $F = x'z + yz$
 - $F' = (x'z + yz)'$
- DeMorgan's
 - $F' = (x'z)' (yz)'$
- DeMorgan's
 - $F' = (x''+z')(y'+z')$
- Reduction -> eliminate double negation on x
 - $F' = (x+z')(y'+z')$



This format is called product of sums

Conversion Between Canonical Forms

- ° Easy to convert between minterm and maxterm representations
- ° For maxterm representation, select rows with **0's**

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$G = xyz + xyz' + x'yz$$



$$G = m_7 + m_6 + m_3 = \Sigma(3, 6, 7)$$




$$G = M_0 M_1 M_2 M_4 M_5 = \Pi(0, 1, 2, 4, 5)$$




$$G = (x+y+z)(x+y+z')(x+y'+z)(x'+y+z)(x'+y+z')$$

Representation of Circuits

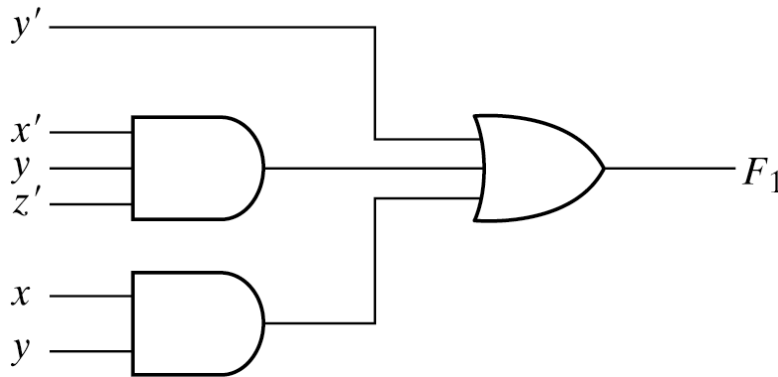- All logic expressions can be represented in 2-level format
- Circuits can be reduced to minimal 2-level representation
- Sum of products representation most common in industry.



(a) Sum of Products

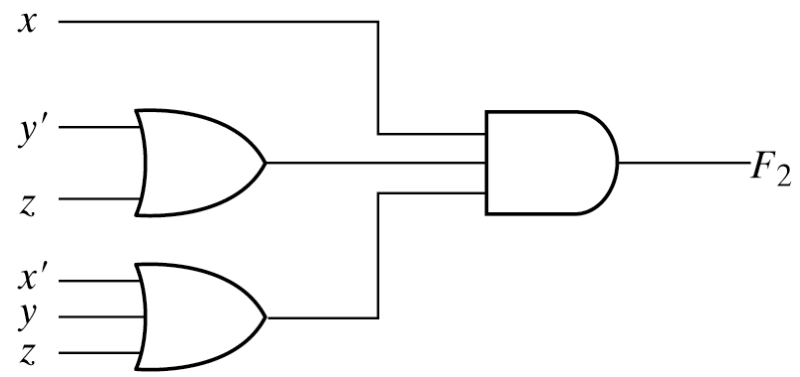

(b) Product of Sums

Fig. 2-3 Two-level implementation

Summary

- Truth table, circuit, and boolean expression formats are equivalent
- Easy to translate truth table to SOP and POS representation
- Boolean algebra rules can be used to reduce circuit size while maintaining function
- All logic functions can be made from AND, OR, and NOT
- Easiest way to understand: **Do examples!**
- Next time: More logic gates!